

# Digital Integrated Circuits

Almost all of the digital circuits used in modern digital systems are integrated circuits (ICs).

An integrated circuit is a complete electronic circuit in which both active and passive are fabricated on an extremely tiny single chip of silicon.

Digital ICs are categorized according to the number of basic gates or gate-equivalent circuits that they contain. The commonly used categories and the range of gates of each category are as follows

Number of gates	Integrated cts Category Name	Abbreviation
1 - 12	Small-scale Integration	SSI
13 - 99	Medium-scale "	MSI
100 - 9999	Large-scale "	LSI
10,000 - 99,999	Very large-scale "	VLSI
over 100,000	Ultra-high scale "	UHSI

SSI → simple logic gates

MSI → counters, code converters

LSI/VLSI → microprocessors ICs used as "brains" in computers

UHSI → gates array

## Logic families

Many integrated logic families exist - The most commonly used ones are TTL and CMOS

- TTL (Transistor - Transistor Logic) which uses Bipolar Transistor as its main circuit element



- CMOS (complementary Metal oxide Semiconductor) uses the enhancement - mode MOSFET as its principal circuit element. other also exist:
- RTL (Resistor - Transistor logic) uses Resistor and Transistors
- DTL (Diode Transistor logic) uses Diode and Resistor etc .....

## TTL logic families


Devices in the standard TTL family are identified by numbers that start with 74 or, for military specification 54. Two or three digits after the 74 are used to identify the logic function performed by the device -

Table below shows the identifying numbers and the logic function performed by several commonly available TTL devices


Device number	Description of Device	Number of gates
7400	Quadruple 2 - input NAND gates	4
7402	Quadruple 2 input NOR gates	4
7404	Hex Inverters	6
7408	Triple - 2 - input NAND gates	4
7410	Triple - 3 - input NAND gates	3
7420	Dual 4 - input NAND gates	2
7430	8 - input NAND gates	1
7432	Quadruple 2 - input OR gates	4
7486	Quadruple 2 - input XOR gates	4
7493	4 - bit binary counter	1

Numbers and letters on IC Packages identify the logic family and the logic function they performed. In addition an IC may also have numbers and letters which indicate which company made the device, the year and month, the package type and a code which indicates how thoroughly the device was tested.

Exple

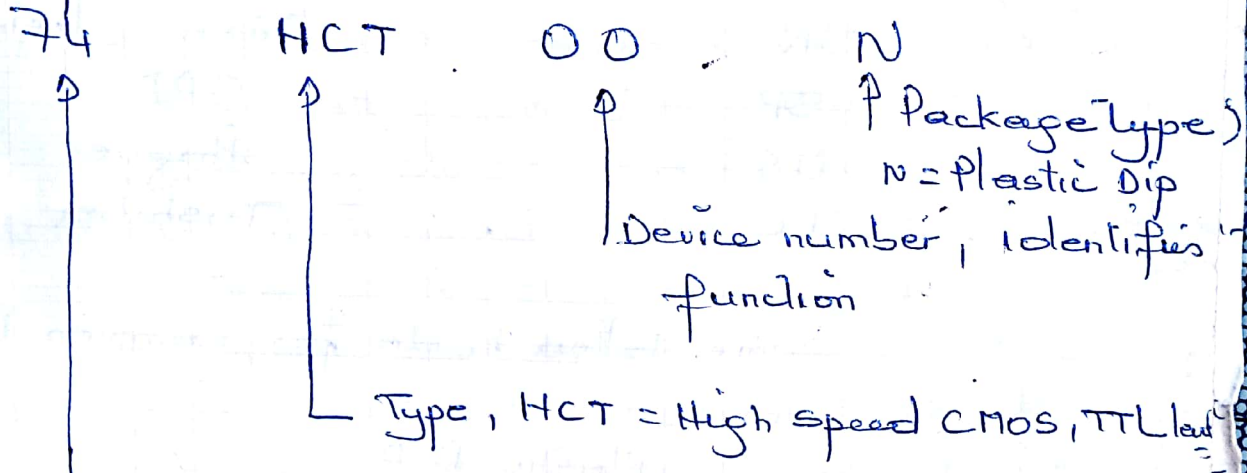

Commercial Temperature range.

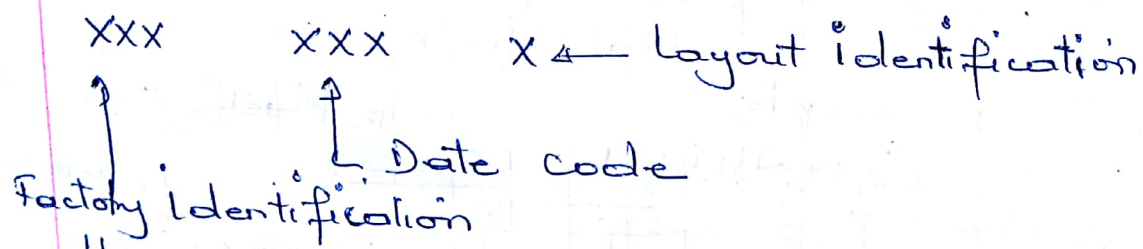

Here are some company codes for the most common IC manufacturers

Code	Manufacturer
AM	Advanced Micro devices
CD	GE/ RCA
DM	National Semiconductor
F	Fairchild
GD	Goldstar
H	Harris
HD	Hitachi
IM	Intersil

2 X  
ex)




KS	Samsung
UR	Sharp
M	SAS
MC	Motorola
MM	Monolithic Memories
MN	Parasonic
N	Signetics
P	Intel
SN	Texas Instruments
SP	SPI
US	Sprague
Tc	Toshiba

Some letters code for common Package type are :

- N — Plastic DIP
- J — Ceramic DIP
- D — Glass / metal DIP
- W — flat pack

Exple

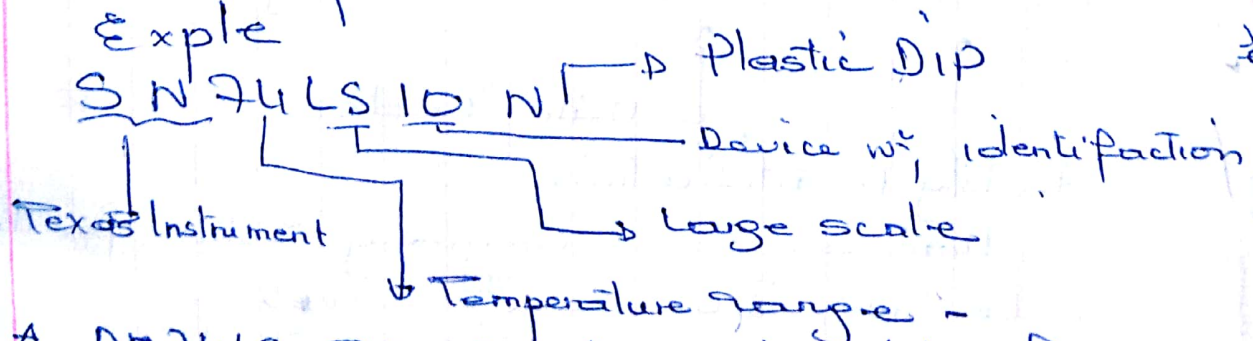

A SN74LS08J can be replaced if faulty by SN74LS08J.

In other words, quality considerations aside you care only about the function of a device not the manufacturer.

## CMOS Logic families

The advantage of logic gates made with MOS transistors is that they dissipate very little power when operated at low frequencies.

Here are some TTL-compatible subfamilies to help you identify the device you find on a circuit board.

74C00 - First TTL-compatible CMOS family. Microwatt power dissipation at low frequencies but very slow compared to TTL.

74HC00: High speed CMOS. Low power dissipation at low frequency operation, but almost as fast as standard TTL.

74HCT00: Another high speed CMOS. Has input and output voltage levels that are more compatible with TTL.

The first CMOS logic subfamily to be developed was the 4000A Series. The family includes logic functions such as those shown for TTL in the table above, but the devices are numbered differently - for example 4001A contains four 2-input NOR gates etc....

## Characteristics of logic families.

The characteristics are:

- speed
- fan in
- fan out
- noise immunity
- power dissipation

fan out low/high 
$$= \frac{I_{OL}(\max)}{I_{IL}(\max)} = \frac{I_{OH}(\max)}{I_{IH}(\max)}$$

$$V_{NH} = V_{OH}(\min) - V_{IH}(\min)$$
$$V_{NL} = V_{IL}(\max) - V_{OL}(\max)$$




**Speed:** of a logic gate is the time that elapse between the application of a signal to an input terminal and the resulting change in logical state at the output.

**Fan-in:** of a logic gate is the number of inputs (coming from similar circuits) that logic gate can handle properly.

**Fan-out:** of a logic gate is the maximum number of similar circuits that this gate can drive reliably.

**noise immunity** is represented by the maximum indicated noise voltage a logic circuit can withstand without a false change in its output state. It is also called noise margin.

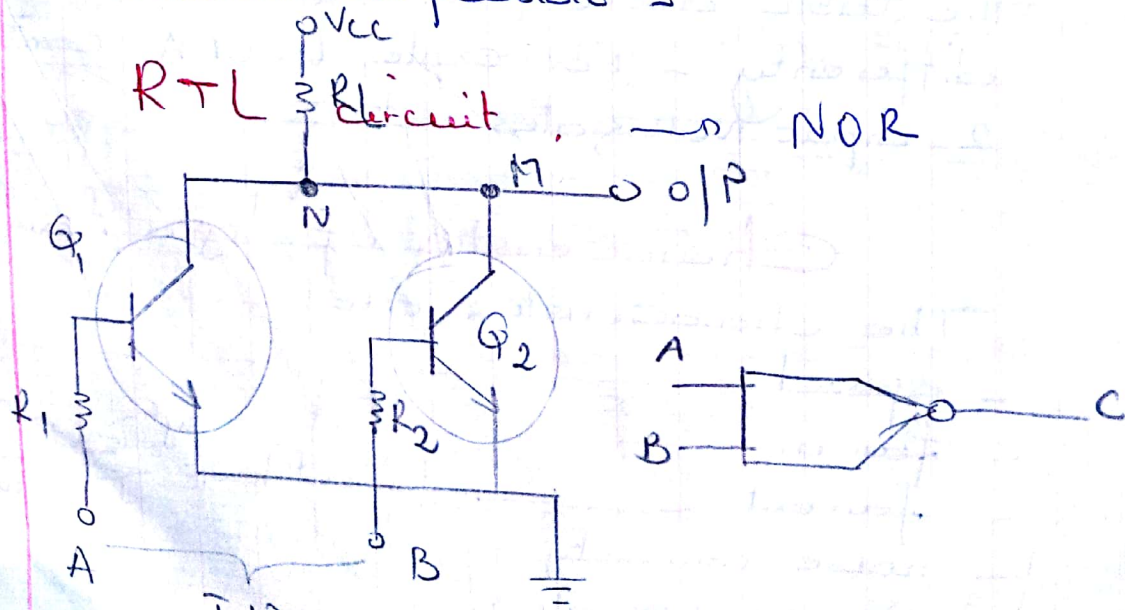**Power dissipation:** is the power dissipated in a circuit as it switches from one state to another and also within all current carrying resistors. Power dissipation of a gate should be as small as possible.



If  $A = B = 0$  (logic 0) both Transistors are off




hence point M goes to  $+V_{CC}$  so that the output is at logic 1.

If either B or A or both terminals are at  $+V_{CC}$  i.e. are high logic (1) both transistors will be fully ON (i.e.) saturate thereby reducing the voltage at point N to 0V. Hence output would be at logic 0.

RTL has the following disadvantages

- 1) low speed
- 2) low fan out - poor noise immunity ....

### DTL circuit

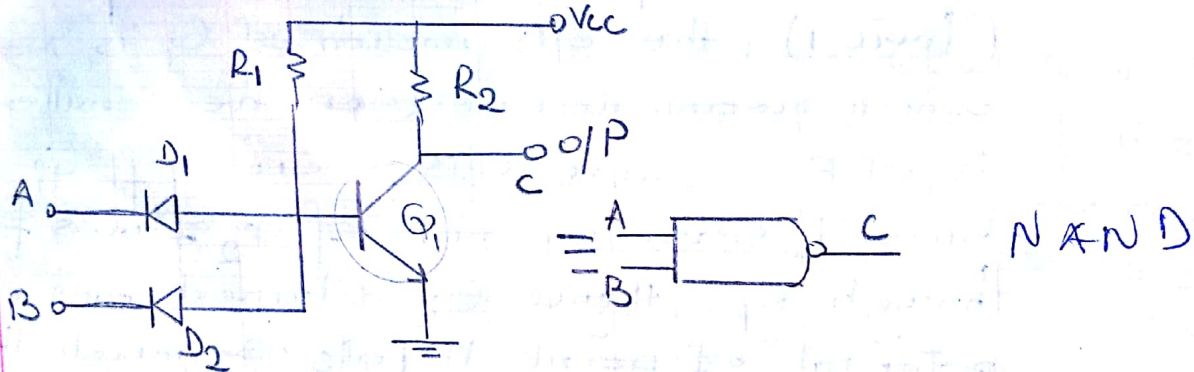


If  $A=B=1$  ( $+V_{CC}$ )  $D_1$  and  $D_2$  are reverse biased and  $Q_1$  is ON so that  $C=0$ .

If either A or B or both are at 0V (logic 0), a conducting diode with cut-off  $Q_1$  and therefore the output should be at logic 1.

DTL has a better noise immunity than RTL because of the 0.7V  $V_{BE}$  of the diodes.

### TTL Circuit (Totem-pole stage).

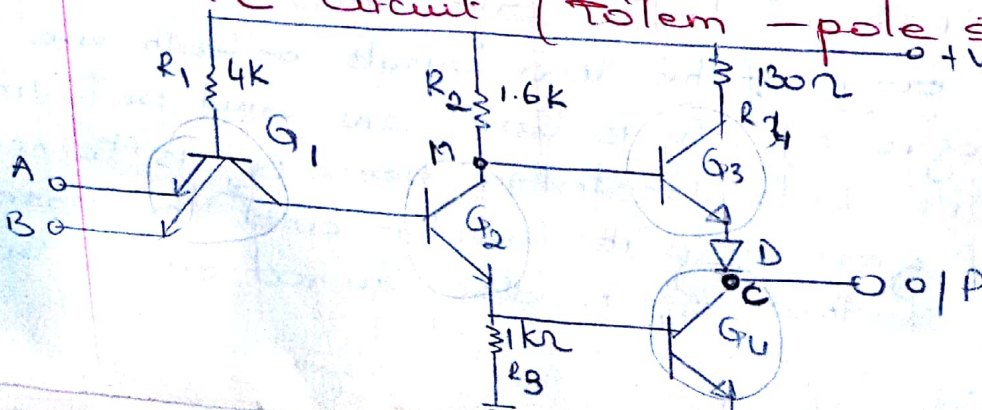



The TTL (Totem-pole) is the most widely used circuit line because of its speed, good fanout and fanin and easy interface with other digital circuitry.

### Circuit operation

$Q_3$ ,  $D$  and  $Q_4$  is often known as totem-pole stage because the three output components are stacked on top of the other in the manner of a totem-pole.

### When Input is high.

When the input terminals have positive voltage (logic 1), the E/B junction of  $Q_1$  is reversed biased which means no current at the emitter hence  $Q_1$  is OFF. Since C/B junction of  $Q_1$  is forward biased base current of  $Q_2$  flows from VCC through  $R_1$  - hence  $Q_2$  is turned ON. As a result potential of point A falls so much that  $Q_3$  is turned OFF. At the same time  $Q_4$  is turned ON by the voltage drop across  $R_3$  - when  $Q_4$  is turned ON, its collector potential (potential at point C) is nearly that of its emitter - hence output is low (at logic 0).

In short when inputs are at logic 1,  $Q_1$  is OFF,  $Q_2$  is ON,  $Q_3$  is OFF and  $Q_4$  is ON and output is at logic 0.

### When Inputs are low

If any of the two inputs or both are low (logic 0),  $Q_1$  is turned ON and potential of its collector falls - hence  $Q_2$  is turned OFF grounding its emitter and the base of  $Q_4$  so that  $Q_4$  is also turned OFF - Since



(56)

$V_{CC}$  is at  $V_{CC}$ , it turns  $Q_3$  ON. The potential of point C is  $V_{CC}$  minus drop in  $R_4$ ,  $Q_3$  and D. which is not much hence output is at logic 1. It may be noted that when even-numbered transistors are ON, the odd-numbered are OFF and vice-versa.

The function of D is to prevent  $Q_3$  and  $Q_4$  from being turned ON simultaneously.

### Input / outputs voltages and currents

The figure below is the manufacturer's data sheet for 5400/7400 NAND gate IC of the Standard TTL Series showing the recommended operating conditions, electrical characteristics and switching characteristics.